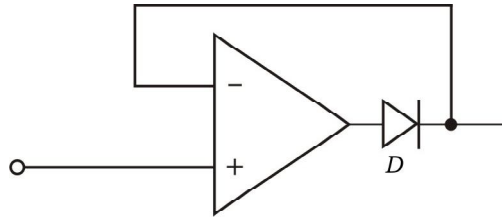


Q.1 To Q.25 carry one mark each.

- Q.1** Which among the given statement is/are CORRECT
 (I) Avalanche breakdown voltage increases with temperature
 (II) Zener breakdown voltage decreases with temperature
 (a) Only I (b) Only II (c) both (d) None

Ans. (c)

- Q.2** If the OPAMP has an open loop gain, $A=100$ and V_r of the diode is $0.7V$; what is the cutin voltage for the superdiode circuit shown below.



- (a) 7 mV (b) 70 mV (c) 700 mV (d) 0.7 mV
Ans. (a)

- Q.3** A BJT is operating in saturation region with $V_{CE} = V_{CE,sat}$ at $20^\circ C$. If the temperature is increased to $40^\circ C$, V_{CE} will

- (a) increase by -5 mV (b) decrease by -5 mV
 (c) decrease by -50 mV (d) not change

Ans. (b)

- Q.4** If h_{FE} is DC current gain $\left(ie\ h_{FE} = \frac{I_C}{I_B}\right)$ and h_{fe} is small signal current gain

$$\left(ie\ h_{fe} = \frac{\partial i_C}{\partial i_B} \Big|_{V_{CE}}\right), \text{ then}$$

- (a) $h_{fe} = h_{FE}$
 (b) h_{fe} is always less than h_{FE}
 (c) h_{fe} is less than h_{FE} for smaller currents and h_{fe} is greater than h_{FE} for larger currents
 (d) h_{fe} is greater than h_{FE} for smaller currents and h_{fe} is less than h_{FE} for larger currents

Ans. (d)

- Q.5** If $X = 0$ in the logic equation

$$[X + Z\{Y + (Z + \bar{X}Y)\}][\bar{Y} + \bar{X}(Z + Y)] = 0 \text{ then}$$

- (a) $Z = 0$ (b) $Z = Y$ (c) $Z = 1$ (d) $Z = \bar{Y}$

Ans. (a)

- Q.6** Minimum no of 2:1 MUX required to implement 2-input OR and 2-input EX-NOR gates are

- (a) 1 and 2 (b) 1 and 3 (c) 2 and 2 (d) 1 and 1


Ans. (d)

- Q.7** Total number of 2-i/P NAND gate required for the implementation of 3 variables Bool-

GATE TEST SERIES - IV (EC)

ean function
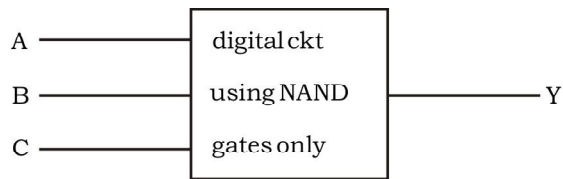
$$Y = f(A, B, C) = \sum m(1, 5, 6, 7) \text{ is}$$



- Ans. (a) 2 (b) 3 (c) 4 (d) 5
(c)

Q.8 In a μP , the service routine for a certain interrupt starts from a fixed location of memory which cannot be used for implementing software break points. The interrupt can be delayed or rejected and it is level triggered. The interrupt can be
 (a) RST 7.5, 6.5 or 5.5 (b) RST 7.5, 6.5, 5.5 or INTR
 (c) RST 6.5, 5.5 or INTR (d) RST 6.5 or 5.5

Ans. **(d)**


Q.9 The ROC of z-transform of the discrete time sequence is

$$x[n] = \left(\frac{1}{4}\right)^n u(n-1) + 5^n u(-n-1)$$

- (a) $\frac{1}{4} < |Z| < 5$ (b) $\frac{1}{5} < |Z| < 4$ (c) $\frac{1}{5} < |Z| < \frac{1}{4}$ (d) $|Z| > 5$

Ans. **(a)**

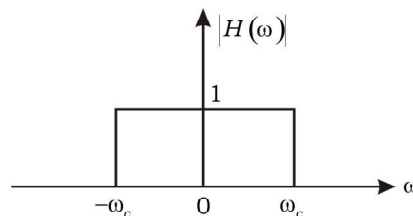Q.10 Given below is the frequency response of an ideal LPF. The LPF is (TI : Time Invariant)



- (a) Linear, TI, Causal (b) Linear, TI & Non-Causal
 (c) Linear, Not TI & Causal (d) Linear, Not TI & Non-Causal

Ans. **(b)**

Q.11 A Fast Fourier Transform (FFT) requires 'M' complex multiplications and 'A' complex additions for computing N-point DFT. Then M & A are

- (a) $M = \frac{N}{2} \log_2 N$; $A = N \log_2 N$ (b) $M = N^2$; $A = N^2 - N$
 (c) $M = N \log_2 N$; $A = N^2$ (d) $M = \frac{N}{2} \log_2 N$; $A = N(N-1)$

Ans. **(a)**

Q.12 Consider the statements regarding a stable and causal minimum phase systems
 (I) All of its poles and zeros lie inside the unit circle.
 (II) Poles must lie inside the unit circle. zeros can lie anywhere.
 (III) The inverse of such system is also stable and causal

GATE TEST SERIES - IV (EC)

(IV) $H(Z) = \left(1 - \frac{1}{2}Z^{-1}\right)$ is a minimum phase system

Which of the above statements is/are CORRECT

- (a) I,III & IV (b) I & III (c) II,III & IV (d) I & IV

Ans. (a)

Q.13 Consider two independent Random Variables 'X' and 'Y' with identical distributions. The 'X' and 'Y' take values 0,1,2 and 3 with probabilities 1/2, 1/4, 1/8 and 1/8. What is the conditional probability $P((X + Y = 4) / |X - Y| = 2)$ is

- (a) 1/32 (b) 1/16 (c) 1/8 (d) 0

Ans. (b)

Q.14 If the Power Spectral density (PSD) for a stationary process is double exponential function $S_y(f) = e^{-\pi|f|}$ Autocorrelation function (ACF) is

- (a) $\frac{1}{1+4\pi f^2}$ (b) $\frac{\pi}{1+f^2}$ (c) $\frac{1/\pi}{1+f^2}$ (d) $\frac{(2/\pi)}{1+4f^2}$

Ans. (d)

Q.15 The Nyquist sampling rate for the signal

$$g(t) = \left[\frac{\sin(200\pi t)}{t} \right] \left[\frac{\sin 300\pi t}{\pi t} \right] \text{ is}$$

- (a) 200 Hz (b) 100 Hz (c) 500 Hz (d) 300 Hz

Ans. (c)

Q.16 given $\mu_0 = 4\pi \times 10^{-7} \text{ H/m}$ and $\epsilon_0 = 8.85 \times 10^{-12} \text{ F/m}$ An air filled rectangular waveguide has inner dimensions of $3\text{cm} \times 1\text{cm}$. The wave impedance of TE_{10} mode of propagation in the waveguide at a frequency of 30 GHz is

- (a) 377Ω (b) 391Ω (c) 382Ω (d) 400Ω

Ans. (c)

Q.17 The \vec{E} field (in V/m) of a plane wave propagating in free space is given by

$$\vec{E} = \hat{x}5 \sin(\omega t - \beta z) + \hat{y}5\sqrt{3} \cos(\omega t - \beta z + \pi/3)$$

The time average power flow density in watts is (η_0 is characteristic impedance of free space)

- (a) $\frac{50}{\eta_0}$ (b) $\frac{100}{\eta_0}$ (c) $\eta_0 50$ (d) $\eta_0 100$

Ans. (a)

Q.18 One end of a loss-less transmission line having the characteristic impedance of 50Ω and length of 2cm is short-circuited. At a frequency of 6 GHz, the input impedance at the other end of the transmission line is


- (a) 0 (b) ∞ (c) Capacitive (d) Inductive

GATE TEST SERIES - IV (EC)

Ans. (c)

NETWORK

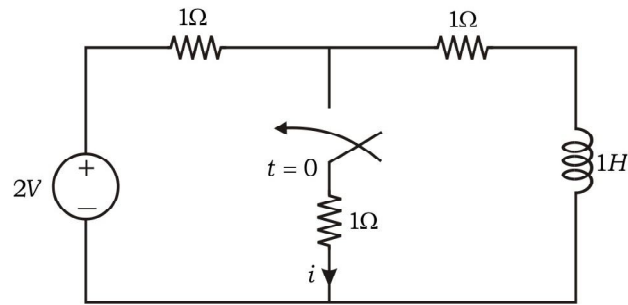Q.19 In the circuit shown, the switch S is closed at $t=0$ after long time. $i(0^+)$ is



(a) 0.5A


(b) 1A

(c) 2A

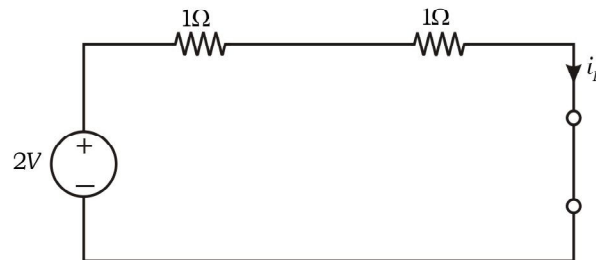(d) 1.5A

Ans. (a)


Exp. $t < 0$ S \rightarrow opened for long time i.e. Steady state $L \rightarrow S/C$



$$\text{So } i_L = \frac{2}{1+1} = 1A$$

$$\text{Hence } i_L(0^+) = i_L(0^-) = 1A$$

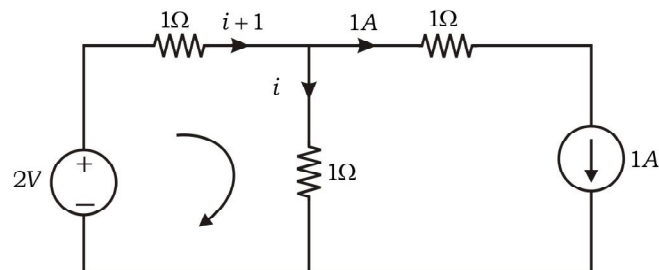$t = 0^+$ S is closed, L as a current source




$$-2 + 1 \cdot (i+1) + i \cdot 1 = 0$$

$$2i = 1 \Rightarrow i = 0.5A$$

GATE TEST SERIES - IV (EC)

Q.20

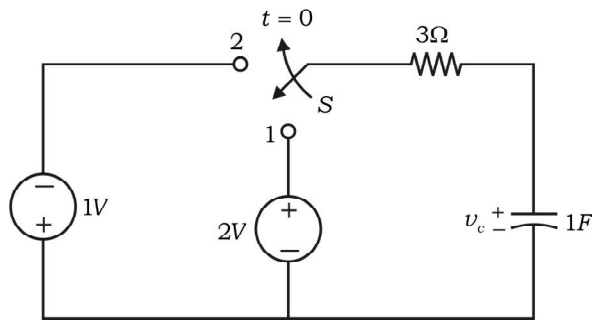


In the above circuit shown S is changed from position 1 to 2, $\frac{dv_c}{dt}(0^+)$ is

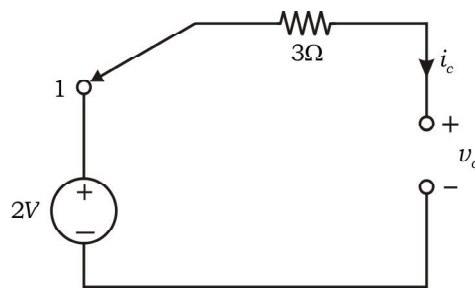- (a) 3V/sec (b) -1V/sec (c) -2V/sec (d) -3V/sec

Ans. (b)


Exp. $S \rightarrow 1$ for long time $t < 0$ C behaves as open circuit in steady state



$$v_c = 2V$$

hence $v_c(0^+) = v_c(0^-) = 2V$

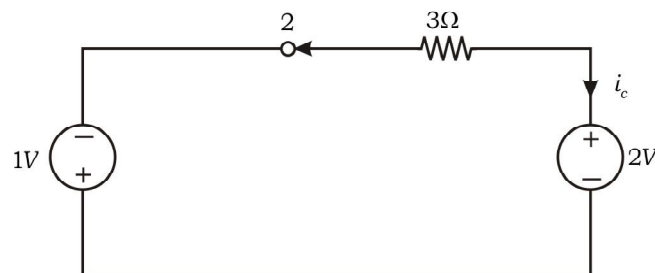At $t = 0^+$ $S \rightarrow 2$ C acts a voltage source of 2V




$$i_c = -\frac{3}{3} = -1A$$

$$i_c(0^+) = -1A$$

$$i_c = C \frac{dv_c}{dt} \Rightarrow i_c(0^+) = 1 \times \frac{dv_c}{dt}(0^+)$$

$$\Rightarrow \frac{dv_c}{dt}(0^+) = -1V / \text{sec}$$

GATE TEST SERIES - IV (EC)

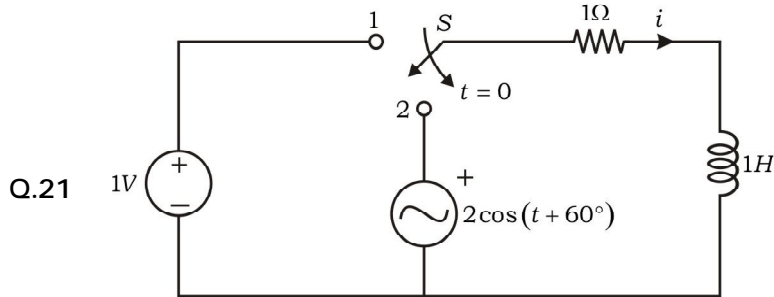


The switch S is changed from 1 to 2 position after long time, $\frac{di}{dt}(0^+)$ is

- (a) 1A/s (b) 0.5A/sec (c) 0 (d) $\frac{\sqrt{3}}{2}$ A/sec

Ans. (c)


Exp. $t < 0$ $S \rightarrow 1$ for long time i.e. Steady state L acts as S/C

$$i = \frac{1}{1} = 1A$$

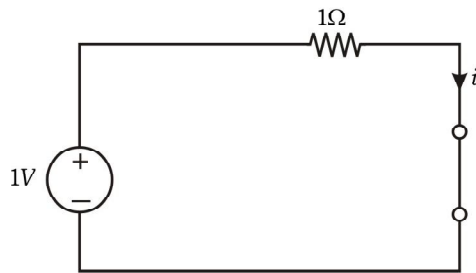

So $i(0^+) = i(0^-) = 1A$

At $t \geq 0$ $S \rightarrow 2$

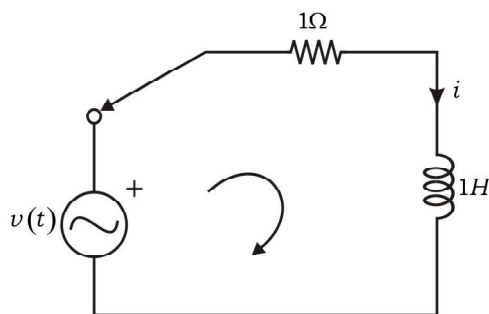

$$i \cdot \frac{di}{dt} + 1 \cdot i = v(t)$$

$$\Rightarrow \frac{di}{dt} = 2 \cos(t + 60^\circ) - i(t)$$

$$\Rightarrow \frac{di}{dt}(0^+) = 2 \cos 60^\circ - i(0^+) = 1 - 1 = 0$$

CONTROL SYSTEM

GATE TEST SERIES - IV (EC)

Q.22 The state transition matrices of a system at instant $t=2$ & $t=3$ are given as

$$\phi(2) = \begin{bmatrix} 2 & 0 \\ 0 & -3 \end{bmatrix} \quad \& \quad \phi(3) = \begin{bmatrix} -4 & 0 \\ 0 & 5 \end{bmatrix}$$

(a) $\begin{bmatrix} -2 & 0 \\ 0 & 2 \end{bmatrix}$

(b) $\begin{bmatrix} -2 & -3 \\ -3 & 2 \end{bmatrix}$

(c) $\begin{bmatrix} -8 & 0 \\ 0 & -15 \end{bmatrix}$

(d) $\begin{bmatrix} 0 & 8 \\ 15 & 20 \end{bmatrix}$

Ans. (c)

Exp.

As $\phi(t) = e^{At}$

$$\phi(t_1 + t_2) = e^{A(t_1+t_2)} = e^{At_1} e^{At_2} = \phi(t_1)\phi(t_2)$$

$$\phi(5) = \phi(2+3) = \phi(2)\phi(3)$$

$$= \begin{bmatrix} 2 & 0 \\ 0 & -3 \end{bmatrix} \begin{bmatrix} -4 & 0 \\ 0 & 5 \end{bmatrix} = \begin{bmatrix} -8 & 0 \\ 0 & -15 \end{bmatrix}$$

Q.23 A system having T.F. $\frac{1}{s+1}$ is excited by a step function of magnitude '3'. The time required by output to reach upto 96% of its steady state value is

(a) 0.54 sec

(b) 1.23 sec

(c) 2.08 sec

(d) 3.22 sec

Ans. (d)

Exp.

Input = $3u(t)$

$$R(s) = 3/s$$

$$G(s) = \frac{C(s)}{R(s)} = \frac{1}{s+1}$$

$$C(s) = \frac{3}{s(s+1)} = \frac{3}{s} - \frac{3}{s+1}$$

$$\Rightarrow c(t) = 3(1 - e^{-t})$$

$$t \rightarrow \infty \quad c_{SS} = 3$$

At $t = T_1$, $c = 0.96c_{SS}$

$$= 0.96 \times 3$$

so $0.96 \times 3 = 3(1 - e^{-T_1})$

$$\Rightarrow T_1 = 3.22s$$

MATHEMATICS

Q.24 If eigen values of $A_{3 \times 3}$ matrix are $-1, 1/2, 3$. The eigen values of $A^2 + 2A + I$ are

(a) 0, 16, 9/4

(b) 1, 1/4, 9

(c) 2, 9/2, 4

(d) 2, 3/2, -2

Ans. (a)

Exp.

$$A^2 + 2A + I = A^2 + 2AI + I^2$$

$$= (A + I)^2$$

$$A \rightarrow -1, \frac{1}{2}, 3$$

$$A + I \rightarrow -1+1, \frac{1}{2}+1, 3+1$$

GATE TEST SERIES - IV (EC)

$$= 0, 3/2, 4$$

$$(A + I)^2 \rightarrow 0, 9/4, 16$$

Q.25 The Cauchy's mean value of the functions e^x & e^{-x} between (0,1) is

- (a) $\ln(e-1)$ (b) 0.5 (c) $\ln\left(\frac{e}{e+1}\right)$ (d) 0.334

Ans. (b)

Exp. $f(x) = e^x, g(x) = e^{-x}$

$$a = 0, b = 1$$

Cauchy's mean value $a < c < b$

$$\frac{f'(c)}{g'(c)} = \frac{f(b) - f(a)}{g(b) - g(a)}$$

$$f'(x) = e^x \text{ \& } g'(x) = -e^{-x}$$

$$\frac{e^c}{-e^{-c}} = \frac{e - e^0}{e^{-1} - e^0} = \frac{e - 1}{1/e - 1}$$

$$\Rightarrow -e^{2c} = \frac{e - 1}{(1 - e)/e}$$

$$\Rightarrow -e^{2c} = -e$$

$$\Rightarrow 2c = 1 \quad \Rightarrow \quad c = 0.5$$

Q.26 To Q.55 carry two marks each.

Q.26 Consider a silicon PN junction with equal level of doping on both sides at room temperature with the given parameters

Doping level = $1 \text{ in } 10^8$

Depletion width(total) = $2 \mu\text{m}$

Density of Si = 2.33 g/cm^3

At. wt. of Si = 28.1

Intrinsic Carrier conc = $1.5 \times 10^{10} \text{ cm}^{-3}$

Permittivity of free space = $8.85 \times 10^{-12} \text{ F/m}$

Dielectric Constant of Si = 12

The peak electric field in the device is

- (a) 75.3 kV/cm from N to P (b) 75.3 kV/cm from P to N
 (c) 150 kV/cm from N to P (d) 150 kV/cm from P to N

Ans. (a)

Q.27 $x[n]$ is a real-valued causal sequence with

$$x[0] > 0 \text{ and } |X(e^{j\omega})|^2 = (1 + a^2) - 2a \cos \omega$$

Then $x[n]$ is

- (a) $\delta[n] - a\delta[n-1]$ (b) $a\delta[n] + \delta[n-1]$
 (c) $a\delta[n] - \delta[n-1]$ (d) $\delta[n] + a\delta[n-1]$

GATE TEST SERIES - IV (EC)

Ans. (a)

Q.28 DTFT of the two-sided sequence

$$x[n] = \left(\frac{1}{4}\right)^{|n|} \text{ is}$$

(a) $\frac{\left(\frac{15}{16}\right)}{\left(\frac{17}{16}\right) - 2\cos\omega}$

(b) $\frac{\left(\frac{17}{16}\right)}{\left(\frac{15}{16}\right) + 2\cos\omega}$

(c) $\frac{15}{17 - 6\cos\omega}$

(d) $\frac{15}{15 - 10\cos\omega}$

Ans. (a)

Q.29 The Z-transform of a sequence is

$$X(z) = \frac{z + 2z^{-2} + z^{-3}}{1 - 3z^{-4} + z^{-5}}$$

If R.O.C includes the unity circle, then DTFT of $x(n)$ at $\omega = \pi$ is

- (a) 1 (b) -1 (c) 0 (d) 2


Ans. (c)

Q.30 If $x[n] = \{1, 2, 3, 3\}$ and $h[n] = \{1, -1, 1\}$ then the circular convolution of $x[n]$ & $h[n]$ is

- (a) $\{2, 0, 4, 1\}$ (b) $\{1, 0, 2, 4\}$ (c) $\{3, 1, 0, 2\}$ (d) $\{1, 4, 2, 2\}$

Ans. (d)

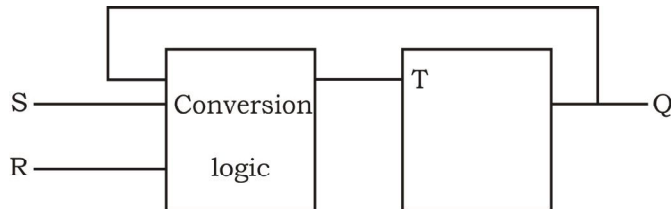Q.31 An SR flip-flop is to be implemented using T-flip flop. The conversion logic should be




- (a) $T = S\bar{Q}_n + RQ_n$ (b) $T = \bar{S}\bar{Q}_n + RQ_n$
 (c) $T = S + \bar{R}Q_n$ (d) $T = SQ_n + R\bar{Q}_n$

Ans. (a)

Q.32 The logic function implemented by the given circuit at terminal out is

GATE TEST SERIES - IV (EC)

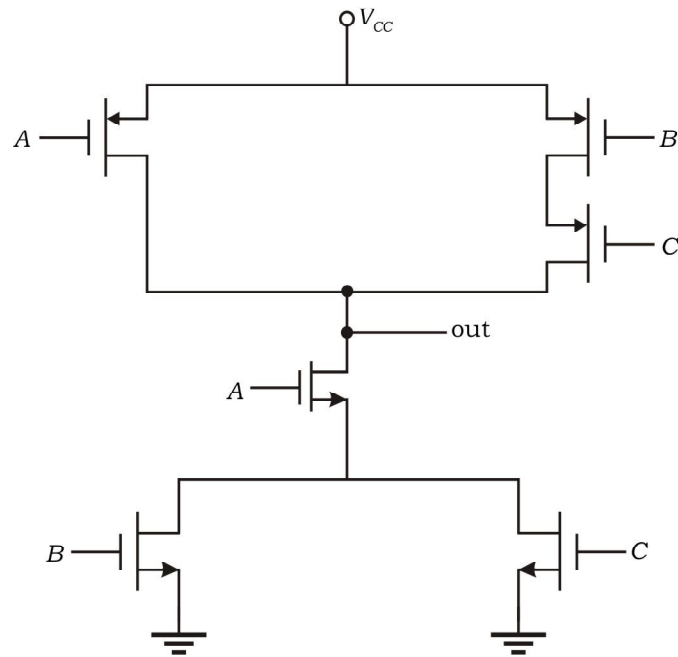

- (a) $\overline{A + BC}$ (b) $A + BC$ (c) $\overline{A.(B + C)}$ (d) $A.(B + C)$

Ans. (a)

Q.33 Following is the segment of 8085 Assembly language program

```
LXI SP, 3FFFH
CALL 2700H
2700H : LXI H, 2050H
        XRA A
        PUSH PSW
        POP H
        SPHL
        POP PSW
        RET
```


On completion of RET instruction, the contents of SP is

- (a) 0046_H (b) 0048_H (c) 2054_H (d) 3FFF_H

Ans. (b)

Q.34 A 100 kHz carrier of 10V amplitude and a 1 kHz modulating signal of 1V amplitude are fed to a balanced modulator. The output of the modulator is passed through an ideal HPF with cut off freq. of 100 kHz. The o/p of the filter is added with 100 kHz signal of 10V amplitude and 90° phase shift as shown in fig. The envelope of the resultant signal is

GATE TEST SERIES - IV (EC)

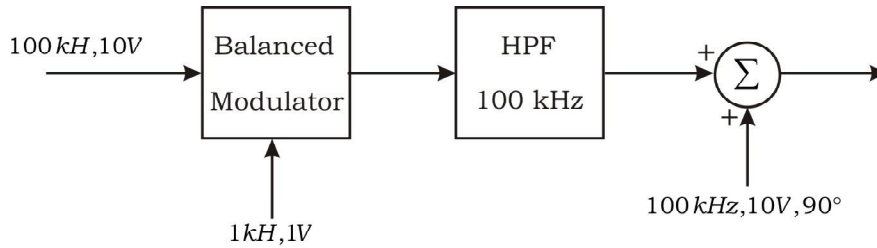

(a) Constant

(b) $5\sqrt{1/4 - \sin(2\pi \times 10^3 t)}$

(c) $10\sqrt{\left(\frac{5}{4}\right) - \sin(2\pi \times 10^3 t)}$

(d) $10\sqrt{\left(\frac{5}{4}\right) + \sin(2\pi \times 10^3 t)}$

Ans. (c)

Q.35 Let X and Y be two statistically independent Random Variables uniformly distributed in the ranges (0, 1) and (2, 6) respectively

Let $Z = X + Y$. Then the probability that $(Z \leq 5)$ is

(a) 1


(b) 5/8

(c) 3/8

(d) 1/2

Ans. (b)

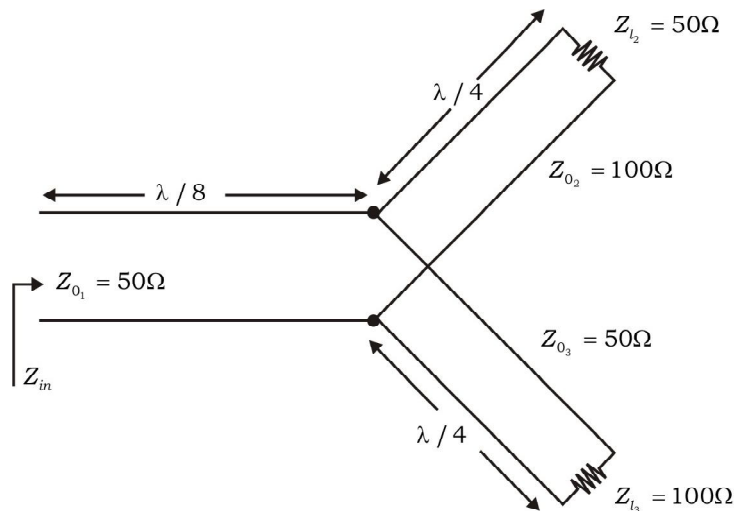Q.36 A transmission line terminates in two branches each of length $\lambda / 4$, as shown. Input impedance Z_{in} , as seen by the source is
(All the transmission lines are lossless)



(a) Inductive

(b) Capacitive

(c) Zero

(d) Infinite

Ans. (a)

Q.37 A plane wave having the electric field component $\vec{E}_i = 10 \cos(2\pi \times 10^9 t - y) \hat{a}_z$ V/m and travelling in free space in incident normally on a loss less medium with $\mu = \mu_0$ and $\epsilon = 4\epsilon_0$ which occupies the region $y \geq 0$. The reflected magnetic field component is given by : ($\eta_0 = 120\pi \Omega$)

(a) $\frac{1}{18\pi} \cos(2\pi \times 10^9 t + y) \hat{a}_x$


(b) $\frac{1}{36\pi} \cos(2\pi \times 10^9 t + y) \hat{a}_x$

(c) $-\frac{1}{18\pi} \cos(2\pi \times 10^9 t - y) \hat{a}_x$

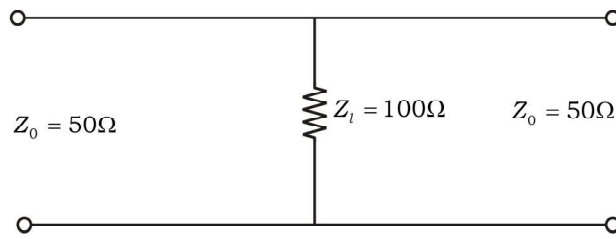(d) $-\frac{1}{36\pi} \cos(2\pi \times 10^9 t - y) \hat{a}_x$

GATE TEST SERIES - IV (EC)

Ans. (b)
Q.38 The S-matrix for the n/w shown below is



- (a) $\begin{bmatrix} -\frac{1}{3} & \frac{2}{3} \\ \frac{2}{2} & -\frac{1}{3} \end{bmatrix}$ (b) $\begin{bmatrix} -\frac{1}{5} & \frac{4}{5} \\ \frac{4}{5} & -\frac{1}{5} \end{bmatrix}$ (c) $\begin{bmatrix} -\frac{1}{2} & \frac{1}{3} \\ \frac{1}{3} & -\frac{1}{2} \end{bmatrix}$ (d) $\begin{bmatrix} 0 & \frac{1}{3} \\ \frac{1}{3} & 0 \end{bmatrix}$


Ans. (b)
Q.39 Consider the given statements regarding smith chart. which among them is/are CORRECT

- (I) An anticlock wise movement on constant 'r' circle adds inductor
 - (II) A circle with origin at centre is constant VSWR circle
 - (III) A clockwise movement of an angle $\pi/2$ means movement on a lossless transmission line towards the generator for a length, $l = \lambda/8$
 - (IV) The smith chart can be used for designing impedance matching network
- (a) I & IV only (b) II, III & IV (c) I, II & III (d) All

Ans. (b)

POWER ELECTRONICS

Q.40

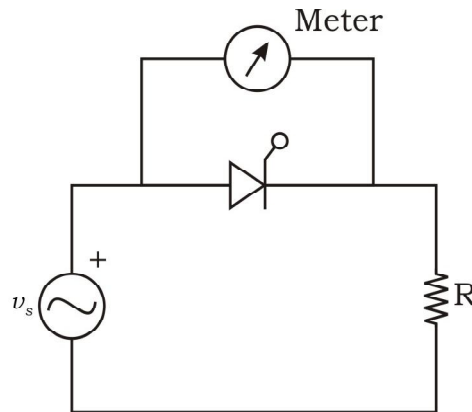

In the above circuit shown, SCR is supplying a pure resistive load from 30 V, 50 Hz supply, if SCR is fired at 45° , the reading of dc voltmeter connected is

(a) 6.5 V (b) 11.5 V (c) 8.1 V (d) 3.2 V

Ans. (b)

Q.41 The ideal SCR's in the full converter are supplying highly inductive load from 5 kHz supply. If the turn off time of each Thyristor is $25 \mu s$. The maximum allowed firing angle is

- (a) 45° (b) 90° (c) 135° (d) 180°

Ans. (c)

NETWORK

GATE TEST SERIES - IV (EC)

Q.42 An input voltage $v(t) = 5\sqrt{2} \sin(t + 20^\circ) + 5\sqrt{2} \sin(2t + 20^\circ)$ is applied to a series combination of resistance of 1Ω and capacitance of $1F$. The steady-state current $i(t)$ in Amp is

- (a) $5 \cos(t + 65^\circ) + 10\sqrt{2} \cos(2t + 65^\circ)$
- (b) $5 \sin(t + 65^\circ) + 10\sqrt{2/5} \sin(2t - 25^\circ)$
- (c) $5 \sin(t - 25^\circ) + 10\sqrt{2} \sin(2t - 25^\circ)$
- (d) $5 \sin(t + 65^\circ) + 10\sqrt{2/5} \sin\{2t + 20^\circ + \tan^{-1}(1/2)\}$

Ans. (d)

Exp. Applied voltage

$$v = v_1 + v_2$$

$$v_1(t) = 5\sqrt{2} \sin(t + 20^\circ)$$


frequency $\omega = 1 \text{ rad/sec.}$, rms $V_1 = 5V$

phase $\bar{V}_1 = 5\angle 20^\circ$

$$v_2(t) = 5\sqrt{2} \sin(2t + 20^\circ)$$


$\omega = 2 \text{ rad/sec}$, rms $V_2 = 5V$

$$\bar{V} = 5\angle 20^\circ V$$

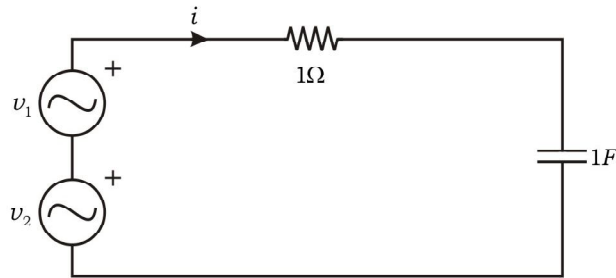

Using super position

If only V_1 is taken

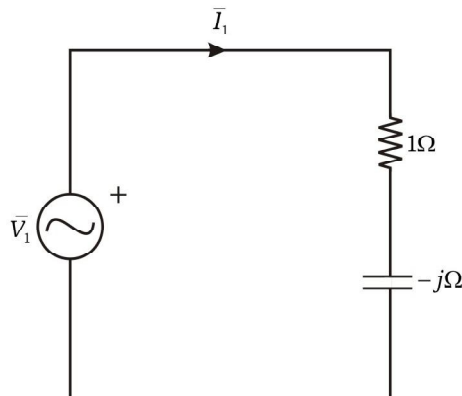

$$Z_{c_1} = \frac{1}{j\omega C_1} = \frac{1}{j \times 1} = -j$$

GATE TEST SERIES - IV (EC)


$$\bar{I} = \frac{\bar{V}_1}{1-j} = \frac{5\angle 20^\circ}{1-j} = \frac{5}{\sqrt{2}} \angle 65^\circ$$

peak $I_{1m} = \frac{5}{\sqrt{2}} \times \sqrt{2} = 5A$

$$i_1(t) = 5 \sin(t + 65^\circ)$$

If only \bar{V}_2 is taken
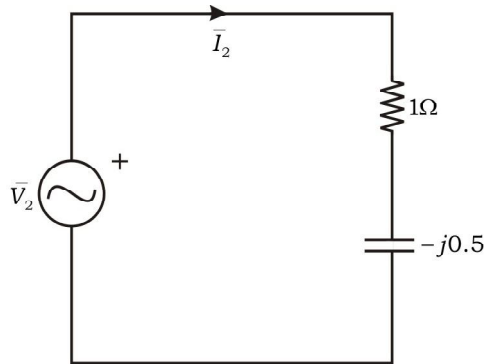
$$Z_{i_2} = \frac{1}{j2 \times 1} = -j0.5$$



$$\bar{I}_2 = \frac{\bar{V}_2}{1-j0.5} = \frac{5\angle 20^\circ}{1-j1/2}$$

$$= \frac{10\angle 20^\circ}{2-j} = \frac{10}{\sqrt{5}} \angle [20^\circ + \tan^{-1}(1/2)]$$

$$rms I_2 = \frac{10}{\sqrt{5}}$$

peak $I_{2m} = \sqrt{2} \times \frac{10}{\sqrt{5}} = 10\sqrt{\frac{2}{5}}$

$$i_2(t) = 10\sqrt{\frac{2}{5}} \sin[2t + 20^\circ + \tan^{-1}(1/2)]$$

so $i(t) = i_1(t) + i_2(t)$

$$\Rightarrow i(t) = 5 \sin(t + 65^\circ) + 10\sqrt{\frac{2}{5}} \sin\{2t + 20^\circ + \tan^{-1}(1/2)\}$$

CONTROL

Q.43 The state space representation of a control system are:

$$\dot{x} = -2x_1 - x_2 + 2u$$

$$\dot{x} = 3x_1$$

$$y = 2x_1 + u$$

(a) Controllable & Observable

(b) Controllable but not observable

(c) Observable but not Controllable

(d) Neither controllable nor Observable

Ans. (a)

Exp.

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} -2 & -1 \\ 3 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 2 \\ 0 \end{bmatrix} u$$

$$y = \begin{bmatrix} 2 & 0 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + [1]u$$

$$A = \begin{bmatrix} -2 & -1 \\ 3 & 0 \end{bmatrix}, B = \begin{bmatrix} 2 \\ 0 \end{bmatrix}, C = [2 \ 0]$$

number of state variables $n=2$

Controllability Test Matrix

$$Q_c = [B \ : \ AB]$$

$$AB = \begin{bmatrix} -4 \\ 6 \end{bmatrix}$$

$$Q_c = \begin{bmatrix} 2 & -4 \\ 0 & 6 \end{bmatrix}$$

rank of $Q_c = 2 = n$ so it is controllable

Observability Test Matrix $Q_o = \begin{bmatrix} C \\ CA \end{bmatrix}$

$$CA = [-4 \ -2]$$

$\Rightarrow Q_o = \begin{bmatrix} 2 & 0 \\ -4 & -2 \end{bmatrix}$ rank of $Q_o = 2 = n$ it is Observable

Q.44 The characteristic equation of a control system is given as

$$s^5 + s^4 + 3s^3 + 3s^2 + 5s + 4 = 0$$

The number of roots lying in right half of s-plane and the number of roots on $j\omega$ axis are

(a) 4 & 2

(b) 2 & 0

(c) 0 & 4

(d) 0 & 2

Ans. (b)

Exp.

$$\begin{array}{l|ll} s^5 & 1 & 3 \ 5 \\ s^4 & 1 & 3 \ 4 \\ s^3 & 0(\varepsilon) & 1 \ 0 \\ s^2 & \frac{3\varepsilon - 1}{\varepsilon} & 4 \ 0 \\ s^1 & \frac{-1 + 3\varepsilon - 4\varepsilon^2}{-1 + 3\varepsilon} & 0 \ 0 \\ s^0 & 4 & 0 \ 0 \end{array}$$

As $\varepsilon \rightarrow 0$ but +ve
1st column

$$\begin{array}{ll}
 1 & +ve \\
 1 & +ve \\
 \varepsilon & +ve \\
 3 - \frac{1}{\varepsilon} = -\infty & -ve \\
 \frac{-1 + 3\varepsilon - 4\varepsilon^2}{-1 + 3\varepsilon} & +ve \\
 4 & +ve
 \end{array}$$

There are 2-sign changes
 so number of roots in RH of s-plane = 2

As complete row is not zero. So no root is lying on $j\omega$ - axis

Q.45 The zero input response of the system,

$$\begin{bmatrix} \dot{x}_1 \\ \dot{x}_2 \end{bmatrix} = \begin{bmatrix} 2 & 0 \\ -1 & -3 \end{bmatrix} \begin{bmatrix} x_1 \\ x_2 \end{bmatrix} + \begin{bmatrix} 1 \\ 0 \end{bmatrix} u$$

Where $\begin{bmatrix} x_1(0) \\ x_2(0) \end{bmatrix} = \begin{bmatrix} 5 \\ 0 \end{bmatrix}$, is

(a) $\begin{bmatrix} e^{-t} \\ e^{2t} \end{bmatrix}$

(b) $\begin{bmatrix} e^{2t} - e^{-3t} \\ e^{2t} + e^{-3t} \end{bmatrix}$

(c) $\begin{bmatrix} e^{-t} - e^{-2t} \\ e^{3t} \end{bmatrix}$

(d) $\begin{bmatrix} 5e^{2t} \\ -e^{2t} + e^{-3t} \end{bmatrix}$

Ans. (d)

Exp.

$$A = \begin{bmatrix} 2 & 0 \\ -1 & -3 \end{bmatrix}, [sI - A] = \begin{bmatrix} s-2 & 0 \\ 1 & s+3 \end{bmatrix}$$

$$\phi(s) = [sI - A]^{-1} = \begin{bmatrix} s-2 & 0 \\ 1 & s+3 \end{bmatrix}^{-1}$$

$$= \frac{1}{(s-2)(s+3)} \begin{bmatrix} s+3 & 0 \\ -1 & s-2 \end{bmatrix}$$

$$\Rightarrow \phi(s) = \begin{bmatrix} \frac{1}{s-2} & 0 \\ -\frac{1}{(s-2)(s+3)} & \frac{1}{s+3} \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{s-2} & 0 \\ -\frac{1}{5(s-2)} + \frac{1}{5(s+3)} & \frac{1}{s+3} \end{bmatrix}$$

Z.I.R $X(s) = \phi(s)x(0)$

$$= \begin{bmatrix} \frac{1}{s-2} & 0 \\ -\frac{1}{(s-2)(s+3)} & \frac{1}{s+3} \end{bmatrix} \begin{bmatrix} 5 \\ 0 \end{bmatrix}$$

$$= \begin{bmatrix} \frac{5}{s-2} \\ -\frac{5}{(s-2)(s+3)} \end{bmatrix} = \begin{bmatrix} \frac{5}{s-2} \\ -\frac{1}{s-2} + \frac{1}{s+3} \end{bmatrix}$$

$$\Rightarrow x(t) = \begin{bmatrix} 5e^{2t} \\ -e^{2t} + e^{-3t} \end{bmatrix}$$

Q.46 The break away point (s) on the root locus of the system with OLTf $\frac{K}{s(s+1)(s+3)}$ is (are)

- (a) K=0.6 (b) K=2.5 (c) K=3.4 (d) K=11

Ans. (a)

Exp. Ch. equation $1 + G(s)H(s) = 0$

$$1 + \frac{K}{s(s+1)(s+3)} = 0$$


$$\Rightarrow s^3 + 4s^2 + 3s + K = 0$$

$$K = -[s^3 + 4s^2 + 3s]$$

For break away point $\frac{dK}{ds} = 0$

$$\frac{dK}{ds} = -[3s^2 + 8s + 3] = 0$$

$$\Rightarrow s = -0.58, -15.42$$

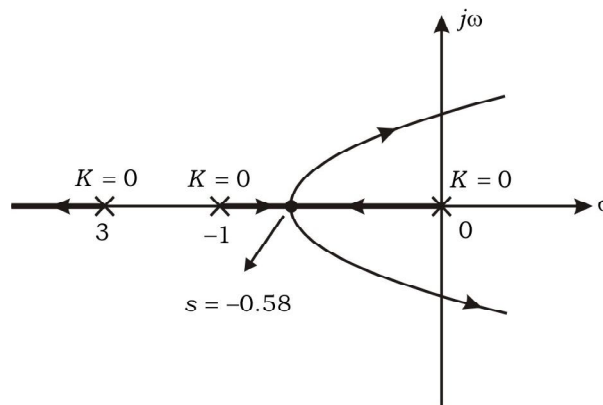

It can be observed from root locu that tywo branches start from $s = 0$ & $s = -1$, so break away point must be in between 0 & 1 i.e. at $s = -0.58$

$$K = -[s^3 + 4s^2 + 3s]$$

$$= -\left[(-0.58)^3 + 4(-0.58)^2 + 3(-0.58)\right]$$

$$= 0.59$$

Q.47 The system with OLTF $G(s)H(s) = \frac{1}{s(s^2 + s + 2)}$ has a gain margin of

- (a) -3 dB (b) 6 dB (c) -6 dB (d) 2 dB

Ans. (b)

Exp. For frequency response $s = j\omega$

$$GH(j\omega) = \frac{1}{j\omega[(2 - \omega^2) + j\omega]}$$

Gain $M = |GH| = \frac{1}{\omega\sqrt{(2 - \omega^2)^2 + \omega^2}}$

phase $\phi = \angle GH = -90^\circ - \tan^{-1}\left(\frac{\omega}{2 - \omega^2}\right)$

At phase cross-over frequency ω_p , $\phi = -180^\circ$

$$-180^\circ = -90^\circ - \tan^{-1}\left(\frac{\omega_p}{2 - \omega_p^2}\right)$$

$$\Rightarrow \tan^{-1}\left(\frac{\omega_p}{2 - \omega_p^2}\right) = 90^\circ$$

$$\Rightarrow 2 - \omega_p^2 = 0 \quad \Rightarrow \quad \omega_p = \sqrt{2}$$

Gain at $\omega_p = \sqrt{2}$

$$M = \frac{1}{\sqrt{2}\sqrt{0 + (\sqrt{2})^2}}$$


$$= \frac{1}{2}$$

G.M. $= \frac{1}{M} = 2$

GM (in dB) $= 20 \log 2 = 6 \text{ dB}$

MATHEMATICS

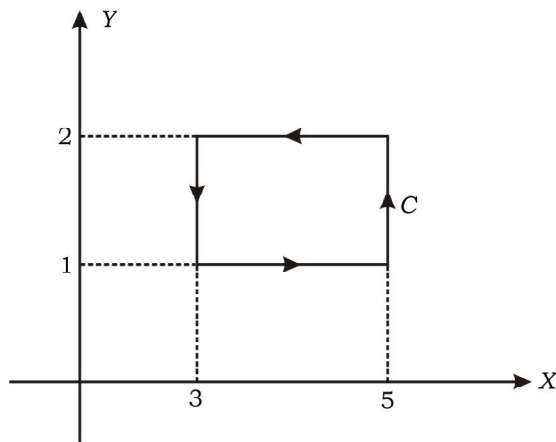Q.48 The Line integral of the vector function $\vec{F} = (x^2 + y^2)\hat{i} + 3xy\hat{j}$ over the path as shown in figure is



- Ans. (a) 3 (b) 0 (c) 2 (d) 6

Exp. $\oint_C \vec{F} \cdot d\vec{r} = \oint_C (x^2 + y^2) dx + 3xy dy$

Where $d\vec{r} = dx \hat{i} + dy \hat{j}$

Using Green's Theorem

$$\begin{aligned} \oint_C (x^2 + y^2) dx + 3xy dy &= \iint_R \left[\frac{\partial}{\partial x} (3xy) - \frac{\partial}{\partial y} (x^2 + y^2) \right] dy dx \\ &= \iint_R (3y - 2y) dy dx \\ &= \iint_R y dy dx \end{aligned}$$

Where R is the region bounded by C

$$\begin{aligned} I &= \int_{x=3}^5 \int_{y=1}^2 y dy dx = \frac{1}{2} \int_{x=3}^5 y^2 \Big|_1^2 dx \\ &= \frac{3}{2} \int_3^5 dx = 3 \end{aligned}$$


Statement for linked Question 49, 50 and 51

Consider the CE amplifier shown below,

$$V_{CC} = 10V ; R_C = 2k ; R_E = 2k ; C_{b_1} = 4\mu F ; C_{b_2} = 8\mu F$$

$$\beta = 100 ; I_{co} = 10nA ; h_{re} = h_{oe} = 0 ; R_s = 3k,$$
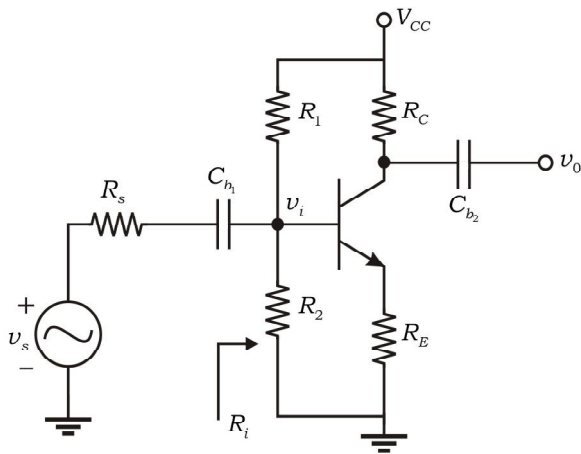
$$R_1 = R_2 = 400k ; V_T = 25mV ; V_{BE} = 0.7V$$



Q.49 The current in the emitter resistance R_E is
 (a) 0.6 mA (b) 1 mA (c) 1.5 mA (d) 2 mA

Ans. (b)

Q.50 The input resistance R_i is
 (a) 3.97 k (b) 200 k (c) 101k (d) 2k

Ans. (c)


Q.51 The small signal voltage gain $\left(\frac{V_o}{V_i}\right)$ is
 (a) -1 (b) -5 (c) -42 (d) -0.5

Ans. (a)

Statement for linked questions 52 & 53

Asymmetric three-level midtread quantizer is to be designed assuming equiprobable occurrence of all quantization levels.

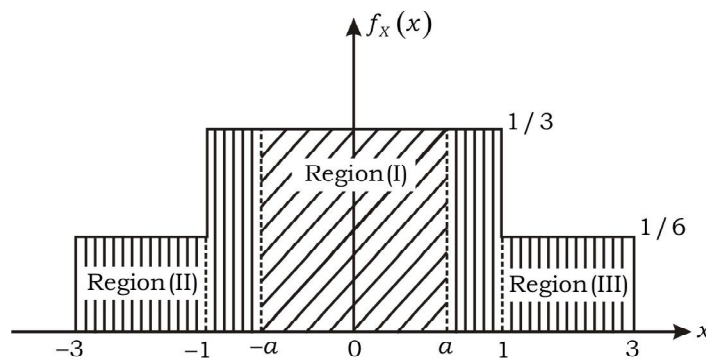Q.52 If the probability density function is divided into three regions as shown in the figure, the value of 'a' in the figure is



(a) 1 (b) 1/2 (c) 1/3 (d) 2/3

Q.53 The Quantization Noise power for the quantization region between '-a' and '+a' in the figure is

(a) 4/81 (b) 1/36 (c) 1/18 (d) 2/81


Ans. (b)

Statement for the linked questions 54 & 55

Consider TTL 2-i/P NAND gate given

GATE TEST SERIES - IV (EC)

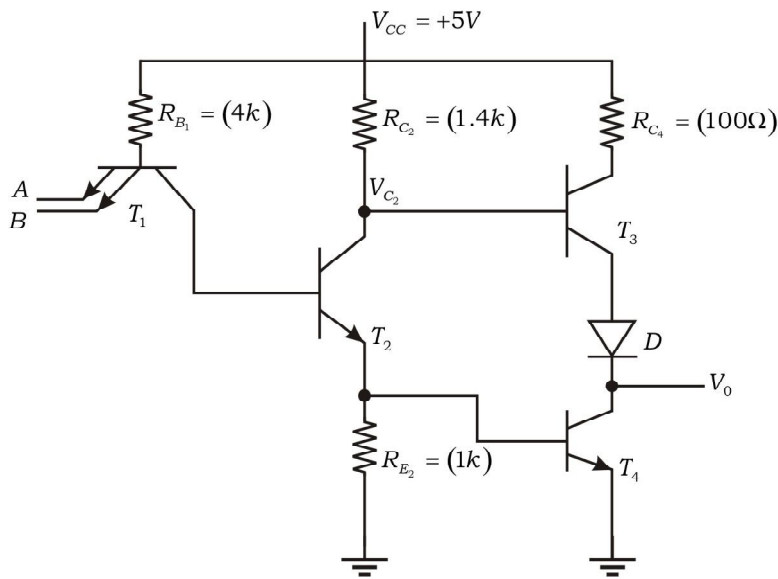$V_{BE,active} = 0.7V$ $V_{BE,sat} = 0.8V$ $V_{CE,sat} = 0.2V$ for each transistor



- Q.54** When $A=B=1$ (ie + 5V) ; the states of the different transistors are
 (a) T_1 : Inverse Active; T_2 : Saturation; T_3 : Saturation T_4 : Saturation
 (b) T_1 : Inverse Active; T_2 : Saturation; T_3 : Cut off; T_4 : Saturation
 (c) T_1 ; Active; T_2 : Cut off; T_3 : Saturation T_4 : Saturation
 (d) T_1 : Active; T_2 : Saturation; T_3 : Cut off; T_4 : Saturation

Ans. (b)

- Q.55** The voltage V_{c2} is equal to

- (a) 0.2V (b) 5V (c) 1.4V (d) 1.0V

Ans. (d)

GENERAL APTITUDE (GA) QUESTIONS

Q. 56 to Q.60 carry one mark each

- Q.56** Four bells ring at the interval of 6,8,12 and 18 seconds. They start ringing together at 12 'O clock. After how many seconds will they ring together again
 (a) 72 (b) 84 (c) 60 (d) 48

Ans. (a)

Exp. It is a question in which you are required to find out the L.C.M. and LCM of 6,8,12 and 18 is 72. Thus the four bells will ring together after 72 seconds.

- Q.57** Choose the most appropriate word from the following options given below to complete the following sentence.

From time to time, those vaccine strains revert to _____, becoming potentially as dangerous as their wild counterparts.

- (a) strategy (b) impermissible
 (c) virulence (d) resolutely

Ans. (c)

- Q.58** Which of the following options given below that is most **opposite** to the given word:

Discrepancy

- (a) contradiction, (b) inconsistency,

GATE TEST SERIES - IV (EC)

Ans. (c) disparity, (d) consensus
(d)

Q59. The question below consists of a pair of related words followed by four pair of words. Select the pair that best expresses the relation in the original pair.

COLOR: SPECTRUM:

- (a) tone : scale (b) sound : waves
(c) verse : poem (d) dimension : space

Ans. (c)

Q60. Choose the most appropriate word from the options given below to complete the following sentence:

In parts of the Arctic, the land grades into the landfast ice so _____ that you can walk off the coast and not know you are over the hidden sea.

- (a) permanently (b) imperceptibly
(c) irregularly (d) precariously

Ans. (b)

Q.61 to Q.65 carry Two marks each

Q.61 The model of development we are pursuing is heavily dependent on the increasing use of energy. Most of the energy currently generated in the world is from non-renewable sources like coal or petroleum. Large tract of the Amazon rain forests are being deforested in order to provide for the increased consumer needs. Are there enough of these non-renewable resources which can allow not only the advanced countries but all people in the world to enjoy an affluent life style? Given the finite nature of these resources, the answer would be no. What about the future generations? Are we going to hand over a depleted earth and multiple problems to them?

According to the author, "what about the future generation"? Means that what would be the solution to this problem:

- (a) Centralized planning (b) Decentralized planning
(c) Sustainable development (d) Economic and environmental development

Ans. (c)

Q.62 With an average speed of 40 km/h train reaches its destination in time. If it goes with an average speed of 35 km/h, it is late by 15 minutes. The length of the entire journey is.

- (a) 40 km (b) 70 km (c) 30 km (d) 80 km

Ans. (b)

Exp. The train needs to travel 15 minutes extra at 35 km/h. Hence it is behind by 8.75 km. The rate of losing distance is 5 km/h. Hence, the train must have travelled for 8.75/5(1 hour 45 minutes) @ 40 km/h. Alternatively you can check with the options.

Q.63 Mohan's expenditure and savings are in the ratio of 3:2. His income increases by 10%. His expenditure increases by 12%. By what percentage does his savings increase.

- (a) 12% (b) 5% (c) 7% (d) 10%

Ans. (c)

Exp. Let his expenditure and savings are Rs. 300 and Rs 200 respectively, so the income is

GATE TEST SERIES - IV (EC)

Rs. 500, which increases to Rs. 550 similarly, the expenditure increases to Rs 336. So the new savings is equal to 214, which is 7% more than Rs 200

- Q.64** An engineer undertakes to build a wall in 50 days. He employs 50 people for the same. However, after 25 days he finds that the work is only 40% complete. How many more men need to be employed to complete the work in time.
(a) 50 (b) 75 (c) 25 (d) 80

Ans. (d)

Exp. In order to finish the work in time engineer needs to finish 60% of work in 25 days.
In print 25 days work does = $20 \times 25 = 1250$ man days (40% of the work)
Hence work left = 60% of the work = 1865 man days since 25 days are left the number of men required is $1875/25 = 75$ men.
50 men are already working so 25 more need to be employed.

- Q.65** There are 20,000 people living in a town out of them 9000 subscribe to times of india and 12,000 to hindustan times. If 4000 subscribe to both how many also not subscribe to any of the two?
(a) 3000 (b) 2000 (c) 1000 (d) 4000

Ans. (a)

Exp. The number of people subscribe both the newspaper have been counted with each so substrates 4000 from each we get the number who read only one of the newspaper.
That means.
5000 read only T 01
8000 read only HT.
Where 4000 read both.
This gives us a total of 17000. Which means 3000 remaining do not read any of the two newspaper